

Assignment 2

**1. Identify all the inputs and outputs for your sequential circuit.**

FSM has 3 states:

- Requires 2 bits:  $y_1, y_0$


Inputs include states and external inputs:

- Current states (2 bits):  $y_1, y_0$
- Start
- Reset
- CMP (if  $a < b$  then  $CMP = 1$ , else  $CMP = 0$ )

Outputs: next states and external outputs

- Next states:  $y_1, y_0$
- Selector for a, selector for x, enable for a, enable for x.

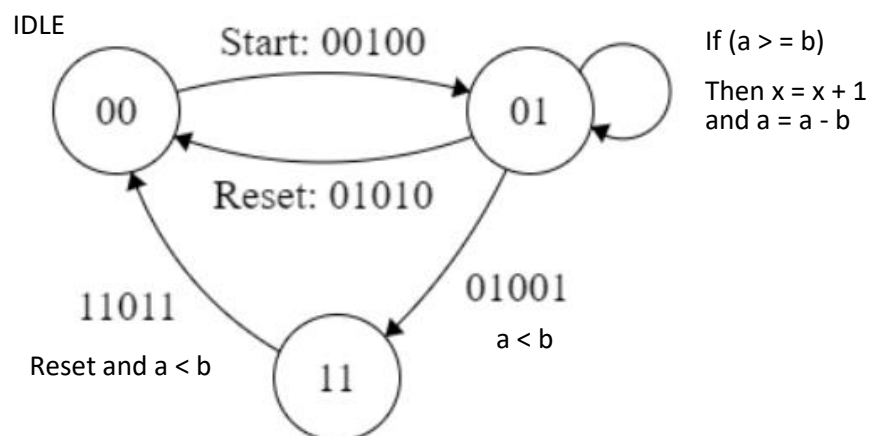**2. Design a finite state machine that will provide the required signals to the circuit in the template.**



**3. Design the combinational logic (or ROM programming) to implement your finite state machine.**

Inputs						Outputs							
Current States		Inputs				Next States			Outputs				
Y1	Y0	Start	Reset	Cmp	0x	Y1	Y0	0x	Ea	Sa	Ex	Sx	0x
0	0	1	0	0	4	0	1	1	1	0	1	0	A
		1	0	1	5	0	1	1	1	0	1	0	A
		Otherwise			X	0	0	0	0	0	0	0	0
0	1	0	0	0	8	0	1	1	1	1	1	1	F
		0	0	1	9	1	1	3	0	0	0	0	0
		0	1	0	A	0	0	0	0	0	0	0	0
		Otherwise			X	0	1	1	0	0	0	0	0
1	1	0	1	1	27	0	0	0	0	0	0	0	0
		otherwise			0	1	1	3	0	0	0	0	0

**4. Implement your design in Logisim. (See file attached)**

- Press and hold Start button until states change in ROM and start the loop.
- Press and hold reset button to restart the circuit, state in ROM goes back to 00.